 


Logic



Learning Objectives

You will be able to:


1. Build truth tables for simple logic gates
2. Build truth tables for simple logic expressions
3. Explain the duality between sets and logic operators
4. Build simple logic circuits in logic.ly

Logic



How do we manipulate 0s and 1s?

Boolean Algebra

 Introduced by an English
Mathematics George
Boole professor while at
University College Cork
in 1854.



Charles Peirce 1886

  


Claude Shannon



[https://www.youtube.com/watch?
v=z7bVw7IMtUg](https://www.youtube.com/watch?v=z7bVw7IMtUg)

Aside: Shannon's Useless Machine

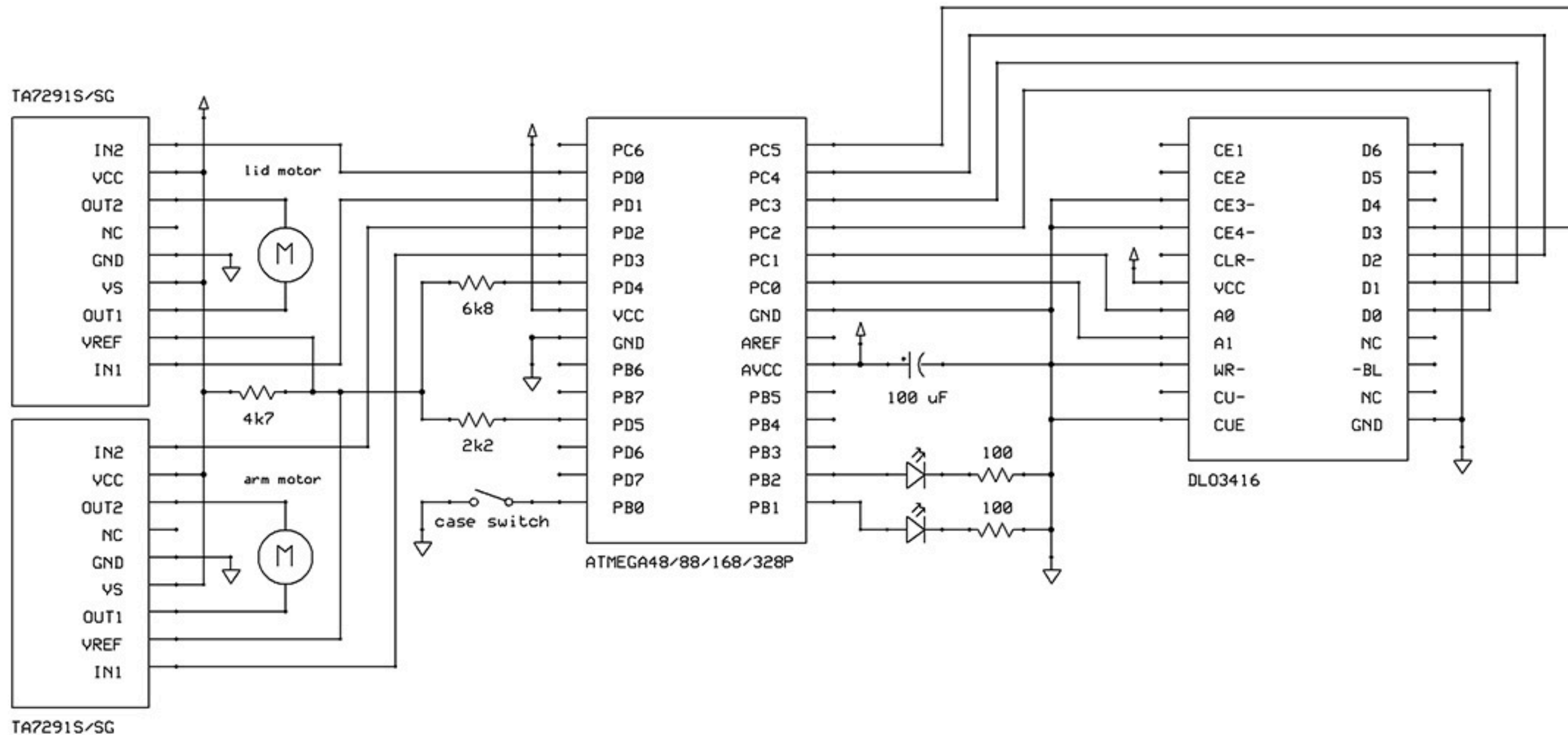

Basic Boolean operations

Values true and false (0 and 1)

Basic operations

And (conjunction), $x \wedge y$, X AND Y

Or (disjunction), $x \vee y$, X OR Y

Not (negation), $\neg x$, NOT X

Implemented using circuits (using logic gates)

Logic is like real life

If it is **dry** AND **warm**
I will go for a run.

Dry	Warm	Run
N	N	N
N	Y	N
Y	N	N
Y	Y	Y

Dry	Warm	Run
0	0	0
0	1	0
1	0	0
1	1	1

If it is **wet** OR **windy**
I will skip school.


Wet	Wind	Skip
N	N	N
N	Y	Y
Y	N	Y
Y	Y	Y

Wet	Wind	Skip
0	0	0
0	1	1
1	0	1
1	1	1


AND

AND	0	1
0	0	0
1	0	1

And in circuits

 

OR

 


OR	0	1
0	0	1
1	1	1

OR gate



Not Gate

 




Output 0 if input 1 and vice versa

Also important

XOR	0	1
0	0	1
1	1	0


NAND	0	1
0	1	1
1	1	0

NOR	0	1
0	1	0
1	0	0

   


Also important


XOR	0	1
0	0	1
1	1	0

 

NAND	0	1
0	1	1
1	1	0

 

NOR	0	1
0	1	0
1	0	0

 

Logical vs Bitwise operations

Logical operators: AND, OR, NOT – performed only a single pair of 0/1 or true/false values

Bitwise operators: AND, OR, NOT, etc, performed on all bits in a value individually, eg

In programming && vs &, || vs |

```

      0110
AND   1110
-----
      0110
  
```

Note: different from addition!!


Note Later

Logic and Sets

AND corresponds to set intersection

Logic \wedge corresponds to Set \cap

$$A \wedge B = A \cap B$$

 


Logic and Sets

OR corresponds to set union


Logic \vee corresponds to Set \cup

$$A \vee B = A \cup B$$

 

$A \cup B$

Truth Table Example

 


Swim on Sunny Days with No Jelly Fish or Big Waves

$$SD \wedge \neg(JF \vee BW)$$

$2 \times 2 \times 2 = 8$ options

SD	JF	B W	JF \vee BW	$\neg(JF \vee BW)$	Swim
1	1	1	1	0	0
1	1	0	1	0	0
1	0	1	1	0	0
1	0	0	0	1	1
0	1	1	1	0	0
0	1	0	1	0	0
0	0	1	1	0	0
0	0	0	0	1	0

Truth Table Example

 

Swim on Sunny Days with No Jelly Fish and No Big Waves

$SD \wedge \neg JF \wedge \neg BW$

SD	JF	B W	$\neg JF$	$\neg BW$	$\neg JF \wedge \neg BW$	Swim
1	1	1				
1	1	0				
1	0	1				
1	0	0				
0	1	1				
0	1	0				
0	0	1				
0	0	0				

De Morgan's Laws

*Not (**A and B**) is the same as Not **A** or Not **B**.*

*Not (**A or B**) is the same as Not **A** and Not **B**.*

De Morgan's Laws apply to sets, propositions, or logic gates, the structure is always the same.

For more see:

<https://brilliant.org/wiki/de-morgans-laws/>

Logic Simulators


Online:

<http://logic.ly/demo/>

<http://academo.org/demos/logic-gate-simulator/>

 Example – half adder

The **half adder** adds two single binary digits A and B . It has two outputs, sum (S) and carry (C).




Exercises:

Write out the truth table for half adder

Simulate on logic.ly/demo

Half adder in logic.ly

 

logic.ly Swim decision

Create a logic.ly simulator to make the Swim decision

Swim on Sunny Days with No Jelly Fish or Big Waves


$$SD \wedge \neg(JF \vee BW)$$

And the other version

$$SD \wedge \neg JF \wedge \neg BW$$

 Example – full adder

accounts for values carried in as well as out



Draw the truth table for full adder

Write the logic functions for S and C_{out}




Flip Flop

A circuit for saving state

A simple memory cell

Simulate using logic.ly

   Use push buttons rather than toggle switches



Other examples

Boolean algebra in search engines

Macaroni AND cheese

Macaroni -cheese

Macaroni OR cheese

Programming (made up language)

If (x==true) AND (y==true)

If (x==true) OR (y==true)

If NOT (x==true)

Short-circuiting

$A \wedge 1$ (and)

$A \vee 1$ (or)

Second argument is executed or evaluated only if the first argument does not suffice to determine the value of the expression

In AND, if first one is 0/false, no need to evaluate other one, as result is always 0/false

In OR, if first one is 1/true, no need to evaluate other one, as result is always 1/true

Optimisation technique

Learning Objectives

Be able to:

Build truth tables for simple logic gates

Build truth tables for simple logic expressions

Explain the duality between sets and logic operators

Build simple logic circuits in logic.ly